

Boolean Algebra

Assignment-2(Session 4)

C++ Class XI

Note : Instruction to submit the assignment

- 1.You have to clearly solve all the given questions.
2. On the first page you have to write your **Name,Class,Email-id,Phone-Number and Assignment number.**
- 3 .Convert the assignment in the PDF form
- 4.Submit your assignment at a given Google form <https://cb.lk/cbjr/cpp-xi>

Q1.Verify each of the boolean expression using truth-table

i) $ABC + A'B + ABC' = B$

ii) $XY + YZ + Y'Z = XY + Z$

iii) $A'BA' + A'BC + A'B'C = A'B + A'C$

Q2.Draw the logic circuit for the expressions given below

i) $Y = (A'.B')'.(C+D)$

ii) $Y = (A+B+C)'.(D+E+F+G)$

iii) $Y = A'B + A.B' + A'B'C$